

## **Sistem de alarmă împotriva incendiilor**

**Nume: Gorgan Raluca-Sara**

**Grupa: 2127**

**Seria: B**

**Profesorii îndrumători: Prof. Dr. Ing. Pop Ovidiu, Dr. Ing. Alexandra Fodor**

## Cuprins

1. Tematica proiectului .....	3
2. Specificatii de proiectare .....	4
3. Schema bloc.....	5
4. Schema electrică a circuitului .....	6
5. Serii de valori standardizate .....	7
6. Oglindă de curent .....	9
7. Repetor .....	15
8. Amplificator operational.....	18
9. Comparator neinversor .....	21
10. LED-ul si rezistența .....	25
11. Releul .....	35
12. Analize Monte Carlo/Worst Case .....	38
13. Bibliografie.....	43

## 1. Tematica proiectului


Să se proiecteze un sistem de alarmă împotriva incendiilor. Știind că senzorul de fum folosit poate să măsoare concentrația de fum liniar în domeniul specificat în tabel în coloana C, sistemul se va proiecta astfel încât alarma să se declanșeze la nivelul de fum menționat în coloana D. Alarma se va opri după ce nivelul de fum scade până la valoarea din coloana E. Senzorul de fum se va modela cu ajutorul unui rezistor. Variația liniară a rezistenței electrice a senzorului cu concentrația de fum este specificată în coloana F și trebuie convertită într-o variație de tensiune în domeniul  $[0 - (VCC - 2V)]$ , VCC fiind precizat în coloana G. Alarma este comandată de un comparator cu histereză prin intermediul unui releu care este modelat cu un rezistor. Starea alarmei (pornit/oprit) este semnalizată de un LED având culoarea specificată în tabel, în coloana H

## 2. Specificatii de proiectare


Tabel : Specificații

C	D	E	F	G	H
Domeniul masurabil al concentrației de fum	Nivelul concentrației de fum pentru pornirea alarmei [ppm]	Nivelul concentrației de fum pentru pornirea alarmei [ppm]	Rezistența senzorului[Ω]	VCC[V]	Culoare LED de semnalizare
1110-1550	1500	1150	2k-12k	14	Roșu

### 3. Schema bloc

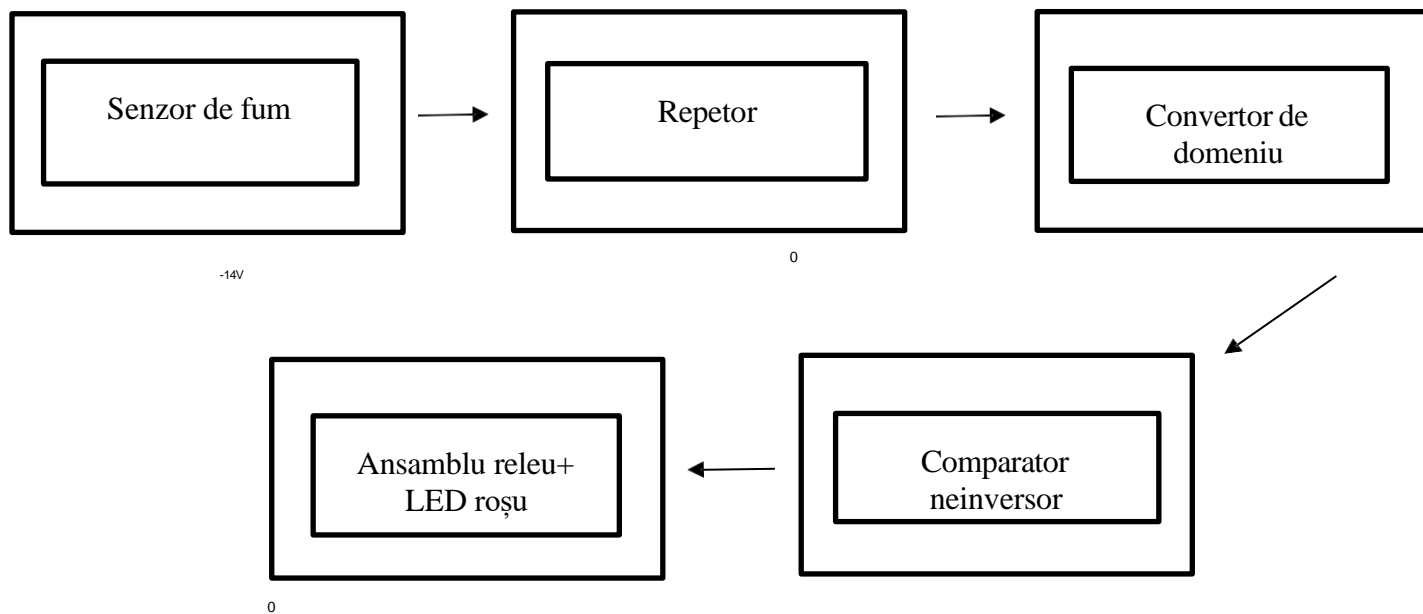

## 4. Schema electrică a circuitului

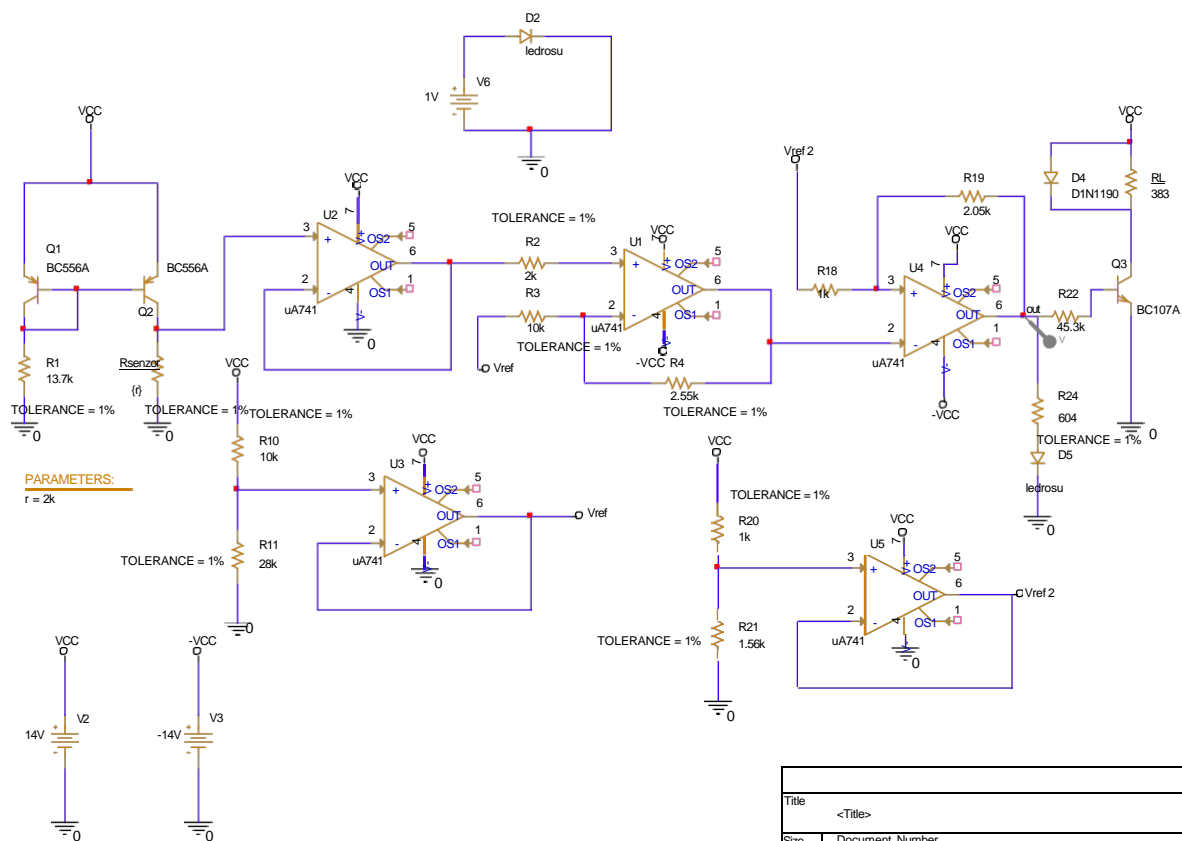

Title	<Title>	Rev	<Rev>
Size	Document Number	Rev	<Rev>
A	<Doc>	Rev	<Rev>
Date:	Friday, May 31, 2024	Sheet	1 of 1

Schema include oglinda de curent, repetorul, amplificatorul operațional, comparatorul neinvertor și ansamblul Releu+LED

## 5. Serii de valori standardizate

Pentru acest proiect am ales rezistente care sa aparțină seriei standardizate E96 cu toleranța de 1%.

Prin urmare, uitandu-mă în tabel, după ce am făcut calculele am realizat următoarele ajustări:

**E-96** ( toleranța 1% )

1.00	2.00	3.01	4.02	5.11	6.04	7.15	8.06	9.09
1.02	2.05	3.09	4.12	5.23	6.19	7.32	8.25	9.31
1.05	2.10	3.16	4.22	5.36	6.34	7.50	8.45	9.53
1.07	2.15	3.24	4.32	5.49	6.49	7.68	8.66	9.76
1.10	2.21	3.32	4.42	5.62	6.65	7.87	8.87	
1.13	2.26	3.40	4.53	5.76	6.81			
1.15	2.32	3.48	4.64	5.90	6.98			
1.18	2.37	3.57	4.75					
1.21	2.43	3.65	4.87					
1.24	2.49	3.74	4.99					
1.27	2.55	3.83						
1.30	2.61	3.92						
1.33	2.67							
1.37	2.74							
1.40	2.80							
1.43	2.87							
1.47	2.94							
1.50								
1.54								
1.58								
1.62								
1.65								
1.69								
1.74								
1.78								
1.82								
1.87								
1.91								
1.96								

R17=13.65K -> 13.7K

R20=1K, R18=1K, R18=1K

$R_{21}=1,56K \rightarrow$

$R_3=10K, R_{10}=10K$

$R_{11}=27.6K \rightarrow 28K$

$R_{19}=2.03K \rightarrow 2.05K$

$R_{24}=600 \text{ Ohm} \rightarrow 604 \text{ Ohm}$

$R_L=378 \text{ Ohm} \rightarrow 383 \text{ Ohm}$

## 6. Oglindă de curent

Pentru a realiza oglinda de curent, mi-am ales tranzistoare pnp low-current de tip BC556A, e important ca tranzistoarele sa fie la fel deoarece se fac pe aceiasi pastila de siliciu si am urmărit foaia de catalog

Philips Semiconductors

Product specification

### PNP general purpose transistors

BC556; BC557

#### FEATURES

- Low current (max. 100 mA)
- Low voltage (max. 65 V).

#### APPLICATIONS


- General purpose switching and amplification.

#### DESCRIPTION

PNP transistor in a TO-92; SOT54 plastic package.  
NPN complements: BC546 and BC547.

#### PINNING

PIN	DESCRIPTION
1	emitter
2	base
3	collector

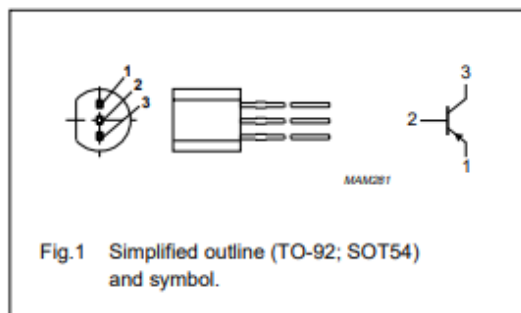

#### LIMITING VALUES

In accordance with the Absolute Maximum Rating System (IEC 134).

SYMBOL	PARAMETER	CONDITIONS	MIN.	MAX.	UNIT
$V_{CBO}$	collector-base voltage	open emitter	—	—80	V
	BC556		—	—50	V
	BC557				
$V_{CEO}$	collector-emitter voltage	open base	—	—65	V
	BC556		—	—45	V
	BC557				
$V_{EBO}$	emitter-base voltage	open collector	—	—5	V
$I_C$	collector current (DC)		—	—100	mA
$I_{CM}$	peak collector current		—	—200	mA
$I_{BM}$	peak base current		—	—200	mA
$P_{tot}$	total power dissipation	$T_{amb} \leq 25^\circ C$	—	500	mW
$T_{stg}$	storage temperature		—65	+150	$^\circ C$
$T_j$	junction temperature		—	150	$^\circ C$
$T_{amb}$	operating ambient temperature		—65	+150	$^\circ C$

cu

specificațiile acestora.



Philips Semiconductors

Product specification

## PNP general purpose transistors

BC556; BC557

### THERMAL CHARACTERISTICS

SYMBOL	PARAMETER	CONDITIONS	VALUE	UNIT
$R_{th\ j-a}$	thermal resistance from junction to ambient	note 1	250	K/W

#### Note

1. Transistor mounted on an FR4 printed-circuit board.

### CHARACTERISTICS

$T_j = 25\text{ °C}$  unless otherwise specified.

SYMBOL	PARAMETER	CONDITIONS	MIN.	TYP.	MAX.	UNIT
$I_{CBO}$	collector cut-off current	$I_E = 0; V_{CB} = -30\text{ V}$	–	–1	–15	nA
		$I_E = 0; V_{CB} = -30\text{ V}; T_j = 150\text{ °C}$	–	–	–4	μA
$I_{EBO}$	emitter cut-off current	$I_C = 0; V_{EB} = -5\text{ V}$	–	–	–100	nA
$h_{FE}$	DC current gain	$I_C = -2\text{ mA}; V_{CE} = -5\text{ V};$ see Figs 2, 3 and 4	125	–	475	
	BC556		125	–	800	
	BC557		125	–	250	
	BC556A		220	–	475	
	BC556B; BC557B		420	–	800	
$V_{CEsat}$	collector-emitter saturation voltage	$I_C = -10\text{ mA}; I_B = -0.5\text{ mA}$	–	–60	–300	mV
		$I_C = -100\text{ mA}; I_B = -5\text{ mA}$	–	–180	–650	mV
$V_{BEsat}$	base-emitter saturation voltage	$I_C = -10\text{ mA}; I_B = -0.5\text{ mA};$ note 1	–	–750	–	mV
		$I_C = -100\text{ mA}; I_B = -5\text{ mA};$ note 1	–	–930	–	mV
$V_{BE}$	base-emitter voltage	$I_C = -2\text{ mA}; V_{CE} = -5\text{ V};$ note 2	–600	–650	–750	mV
		$I_C = -10\text{ mA}; V_{CE} = -5\text{ V};$ note 2	–	–	–820	mV
$C_c$	collector capacitance	$I_E = I_B = 0; V_{CB} = -10\text{ V}; f = 1\text{ MHz}$	–	3	–	pF
$C_e$	emitter capacitance	$I_C = I_E = 0; V_{EB} = -0.5\text{ V}; f = 1\text{ MHz}$	–	10	–	pF
$f_T$	transition frequency	$I_C = -10\text{ mA}; V_{CE} = -5\text{ V}; f = 100\text{ MHz}$	100	–	–	MHz
F	noise figure	$I_C = -200\text{ μA}; V_{CE} = -5\text{ V}; R_S = 2\text{ kΩ};$ $f = 1\text{ kHz}; B = 200\text{ Hz}$	–	2	10	dB

#### Notes

1.  $V_{BEsat}$  decreases by about  $-1.7\text{ mV/K}$  with increasing temperature.
2.  $V_{BE}$  decreases by about  $-2\text{ mV/K}$  with increasing temperature.

### Calculule

$$(R_m \cdot I)_{max} = 12V$$

$$I = \frac{12V}{R_{mmax}} = \frac{12V}{12k\Omega} = 1mA \quad (1)$$

$$R_{min} \cdot I = 2k \cdot 1mA = 2V$$


$$R_{max} \cdot I = 12k \cdot 1mA = 12V$$

$$V_{senzor} \in [2V, 12V]$$



$$I = \frac{V_{cc} - V_{BE}}{R} \Rightarrow R = \frac{V_{cc} - V_{BE}}{I} \quad (2)$$

$$R = \frac{14 - 0,65V}{1mA} = \frac{13,65}{1mA} = 13,65k\Omega \Rightarrow 13,7k\Omega$$

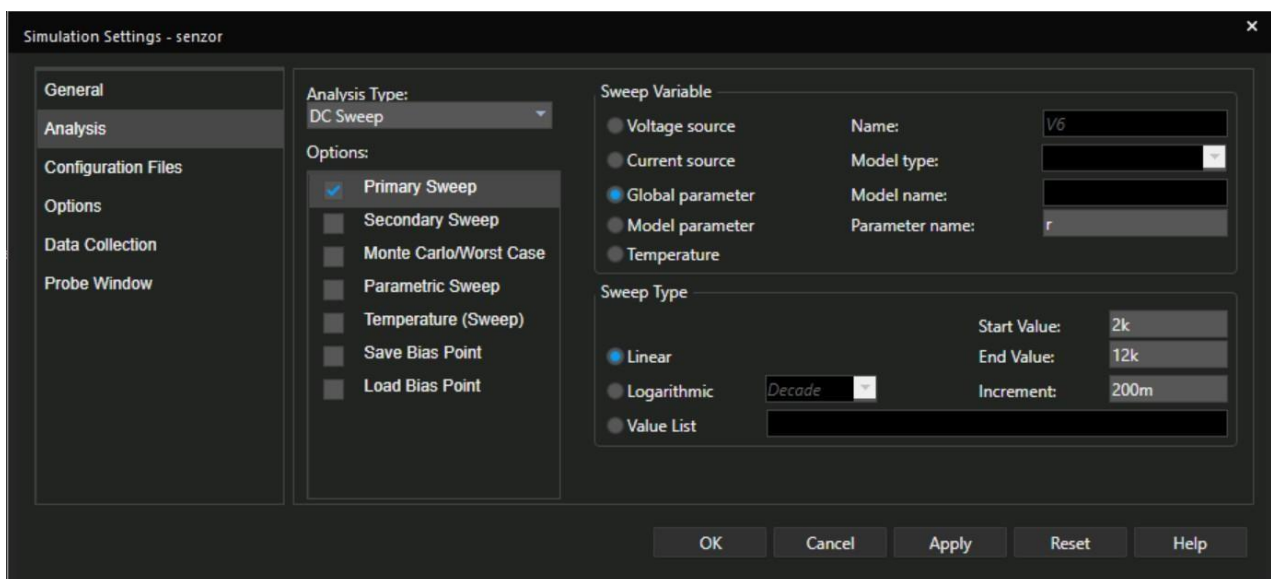
Am realizat o analiză DC Sweep cu parametru global pe care l-am declarat si inițializat.




### Variația curentului

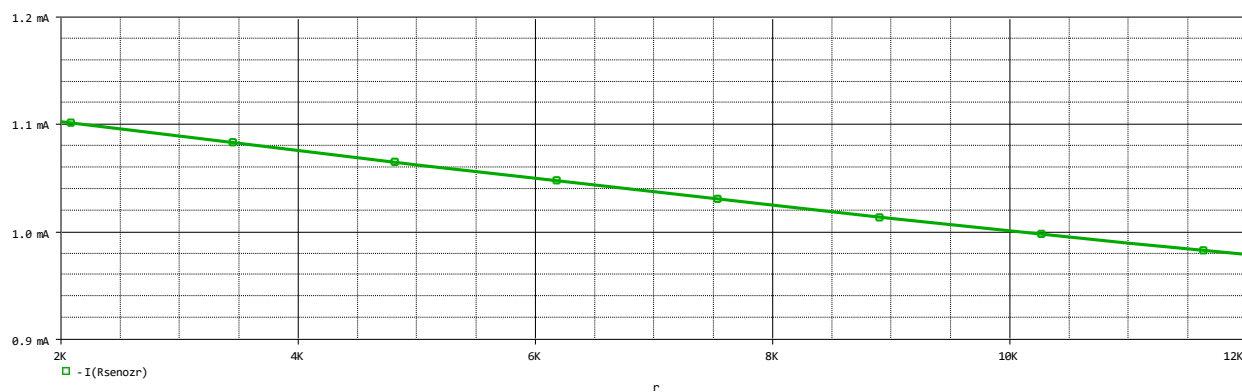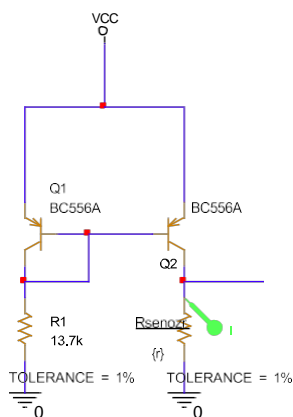

### Variația tensiunii pe senzor

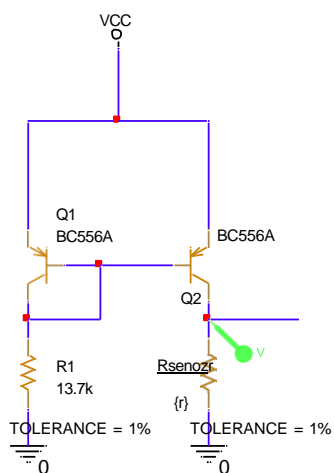

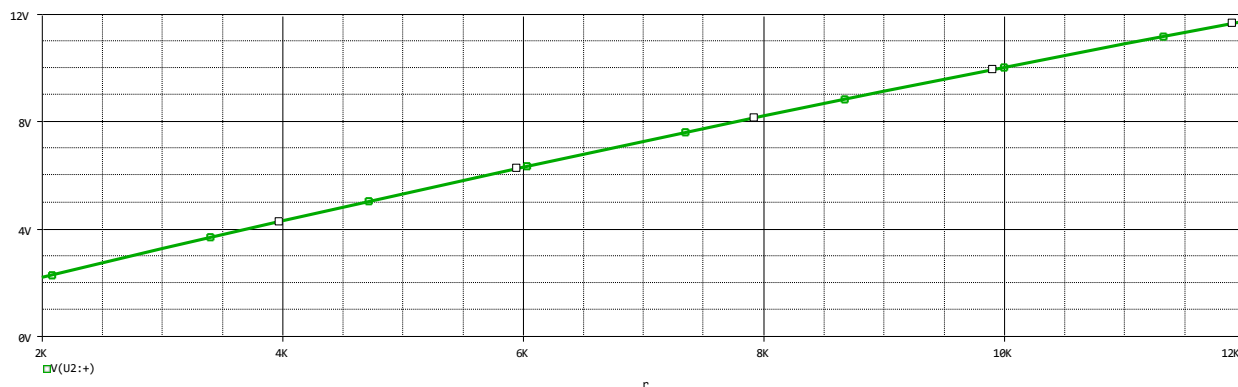

Cu ajutorul formulelor învățate în timpul laboratorului “MIN respectiv MAX” am obținut rezistența minimă și maximă iar apoi cu ajutorul cursorului am obținut exact valoarea acestora.

->MIN=2,20k

->MAX=11,74k

## 7. Repetor

Pentru a realiza repetorul, AO operațional și Comparatorul, am ales amplificatorul operațional  $\mu A741$ , urmărind specificațiile din foaia de catalog.

FAIRCHILD LINEAR INTEGRATED CIRCUITS •  $\mu A741$

$\mu A741A$

ELECTRICAL CHARACTERISTICS ( $V_S = \pm 15V$ ,  $T_A = 25^\circ C$  unless otherwise specified)

PARAMETERS (see definitions)	CONDITIONS	MIN	TYP	MAX	UNITS
Input Offset Voltage	$R_S < 50\Omega$		0.8	3.0	mV
Average Input Offset Voltage Drift				15	$\mu V/^\circ C$
Input Offset Current			3.0	30	nA
Average Input Offset Current Drift				0.5	$nA/^\circ C$
Input Bias Current			30	80	nA
Power Supply Rejection Ratio	$V_S = +10, -20; V_S = +20, -10V, R_S = 50\Omega$		15	50	$\mu V/V$
Output Short Circuit Current		10	25	35	mA
Power Dissipation	$V_S = \pm 20V$		80	150	mW
Input Impedance	$V_S = \pm 20V$	1.0	6.0		M $\Omega$
Large Signal Voltage Gain	$V_S = \pm 20V, R_L = 2k\Omega, V_{OUT} = \pm 15V$	50			V/mV
Transient Response	Rise Time		0.25	0.8	$\mu s$
(Unity Gain)	Overshoot		6.0	20	%
Bandwidth (Note 4)		.437	1.5		MHz
Slew Rate (Unity Gain)	$V_{IN} = \pm 10V$	0.3	0.7		V/ $\mu s$
The following specifications apply for $-55^\circ C < T_A < +125^\circ C$					
Input Offset Voltage				4.0	mV
Input Offset Current				70	nA
Input Bias Current				210	nA
Common Mode Rejection Ratio	$V_S = \pm 20V, V_{IN} = \pm 15V, R_S = 50\Omega$	80	95		dB
Adjustment For Input Offset Voltage	$V_S = \pm 20V$	10			mV
Output Short Circuit Current		10		40	mA
Power Dissipation	$V_S = \pm 20V$			165	mW
	$-55^\circ C$			135	mW
	$+125^\circ C$				
Input Impedance	$V_S = \pm 20V$	0.5			M $\Omega$
Output Voltage Swing	$V_S = \pm 20V, R_L = 10k\Omega$		$\pm 16$		V
	$R_L = 2k\Omega$		$\pm 15$		V
Large Signal Voltage Gain	$V_S = \pm 20V, R_L = 2k\Omega, V_{OUT} = \pm 15V$	32			V/mV
	$V_S = \pm 5V, R_L = 2k\Omega, V_{OUT} = \pm 2V$	10			V/mV

NOTES

- Rating applies to ambient temperatures up to  $70^\circ C$ . Above  $70^\circ C$  ambient derates linearly at  $6.3mW/^\circ C$  for the metal can,  $8.3mW/^\circ C$  for the DIP and  $7.1mW/^\circ C$  for the Flatpak.
- For supply voltages less than  $\pm 15V$ , the absolute maximum input voltage is equal to the supply voltage.
- Short circuit may be to ground or either supply. Rating applies to  $+125^\circ C$  case temperature or  $75^\circ C$  ambient temperature.
- Calculated value from:  $BW(MHz) = \frac{0.35}{\text{Rise Time } (\mu s)}$

FAIRCHILD LINEAR INTEGRATED CIRCUITS •  $\mu A741$


$\mu A741$				
ELECTRICAL CHARACTERISTICS ( $V_S = \pm 15\text{ V}$ , $T_A = 25^\circ\text{C}$ unless otherwise specified)				
PARAMETERS (see definitions)	CONDITIONS	MIN	TYP	MAX
Input Offset Voltage	$R_S < 10\text{ k}\Omega$		1.0	5.0
Input Offset Current			20	200
Input Bias Current			80	500
Input Resistance		0.3	2.0	
Input Capacitance			1.4	
Offset Voltage Adjustment Range			$\pm 15$	
Large Signal Voltage Gain	$R_L > 2\text{ k}\Omega$ , $V_{OUT} = \pm 10\text{ V}$	50,000	200,000	
Output Resistance			75	
Output Short Circuit Current			25	
Supply Current			1.7	2.5
Power Consumption			50	85
Transient Response (Unity Gain)	Rise time		0.3	
	Overshoot		5.0	
Slew Rate	$R_L > 2\text{ k}\Omega$		0.5	

The following specifications apply for  $-55^\circ\text{C} < T_A < +125^\circ\text{C}$ :


Input Offset Voltage	$R_S < 10\text{ k}\Omega$		1.0	5.0
Input Offset Current	$T_A = +125^\circ\text{C}$		70	200
	$T_A = -55^\circ\text{C}$		85	500
Input Bias Current	$T_A = +125^\circ\text{C}$		0.03	0.5
	$T_A = -55^\circ\text{C}$		0.3	1.5
Input Voltage Range		$\pm 12$	$\pm 13$	
Common Mode Rejection Ratio	$R_S < 10\text{ k}\Omega$	70	90	
Supply Voltage Rejection Ratio	$R_S < 10\text{ k}\Omega$		30	150
Large Signal Voltage Gain	$R_L > 2\text{ k}\Omega$ , $V_{OUT} = \pm 10\text{ V}$	25,000		
Output Voltage Swing	$R_L > 10\text{ k}\Omega$	$\pm 12$	$\pm 14$	
	$R_L > 2\text{ k}\Omega$	$\pm 10$	$\pm 13$	
Supply Current	$T_A = +125^\circ\text{C}$		1.5	2.5
	$T_A = -55^\circ\text{C}$		2.0	3.3
Power Consumption	$T_A = +125^\circ\text{C}$		45	75
	$T_A = -55^\circ\text{C}$		60	100

TYPICAL PERFORMANCE CURVES FOR  $\mu A741A$  AND  $\mu A741$

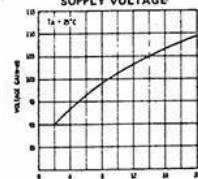
OPEN LOOP VOLTAGE GAIN  
AS A FUNCTION OF  
SUPPLY VOLTAGE




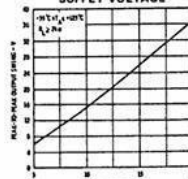OUTPUT VOLTAGE SWING  
AS A FUNCTION OF  
SUPPLY VOLTAGE



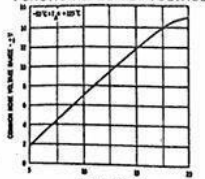
INPUT COMMON MODE  
VOLTAGE RANGE AS A  
FUNCTION OF SUPPLY VOLTAGE



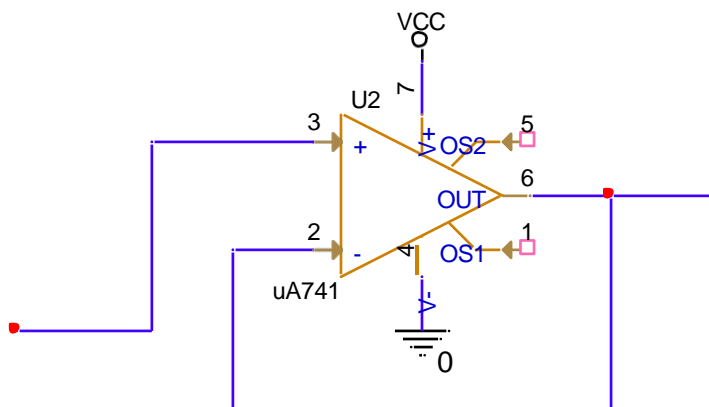


Un amplificator tampon, cunoscut și sub denumirea de buffer, este un circuit electronic folosit pentru a izola etapele unui sistem electronic. Funcția principală a unui amplificator tampon este de a transfera un semnal de la o etapă la alta fără a influența caracteristicile semnalului, cum ar fi amplitudinea sau impedanța.

## 8. Amplificator operațional

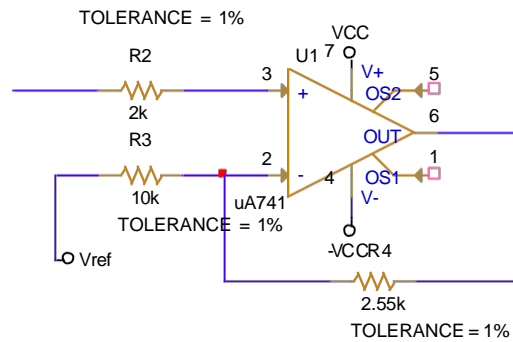

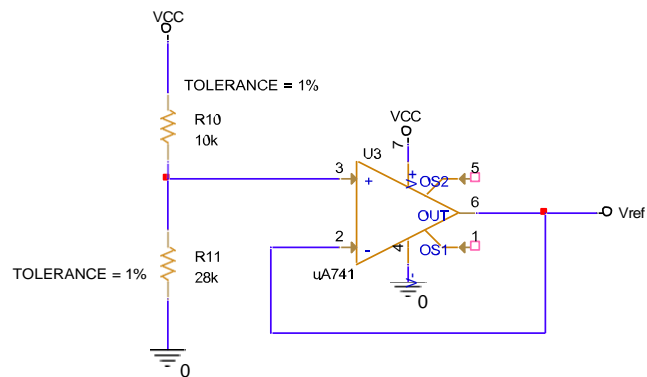Am realizat un divizor de tensiune pentru Vref.





### Calcul

$$\frac{R4}{R3} = \frac{V_{Omax} - V_{Omin}}{V_{cdmax} - V_{cdmin}} \quad (3)$$

$$\frac{R4}{R3} = \frac{12 - 0}{11,74 - 2,20} - 1 \Rightarrow 1,25 - 1 = 0,25$$

$$\frac{R4}{R3} = 0,25$$

Am ales  $R3 = 10k$

$$R4 = 10 \cdot 0,25 \Rightarrow 2,5k$$

În final  $\Rightarrow R3 = 10k$  iar  $R4 = 2,5k$

$$V_{ref} = \frac{(1 + \frac{R2}{R1})}{\frac{R2}{R1}} \cdot \frac{V_{cdmax} - V_{Omax}}{1} \quad (4)$$

$$V_{ref} = \frac{1,25 \cdot 11,74 - 12}{0,26} = \frac{2,675}{0,26} = 10,28V$$

Calcul pentru divizorul de tensiune

$$\frac{R11}{R11 + R10} \cdot V_{CC} = V_{REF} \quad (5)$$

$$\frac{R11}{R11 + R10} \cdot 14 = 10,28V$$

$$\frac{14R11}{R11 + R10} = 10,28V$$

$$14R11 = 10,28R11 + 10,28R10$$

$$14R_{11} - 10,28R_{11} = 10,28R_{10}$$

$$3,72R_{11} = 10,28R_{10}$$

$$\frac{R_{11}}{R_{10}} = \frac{10,28V}{3,72V}$$


$$\frac{R_{11}}{R_{10}} = 2,76$$

Am ales  $R_{10}=10k$

$$\Rightarrow R_{11} = 27,6k \Rightarrow 28k$$


E96 1%

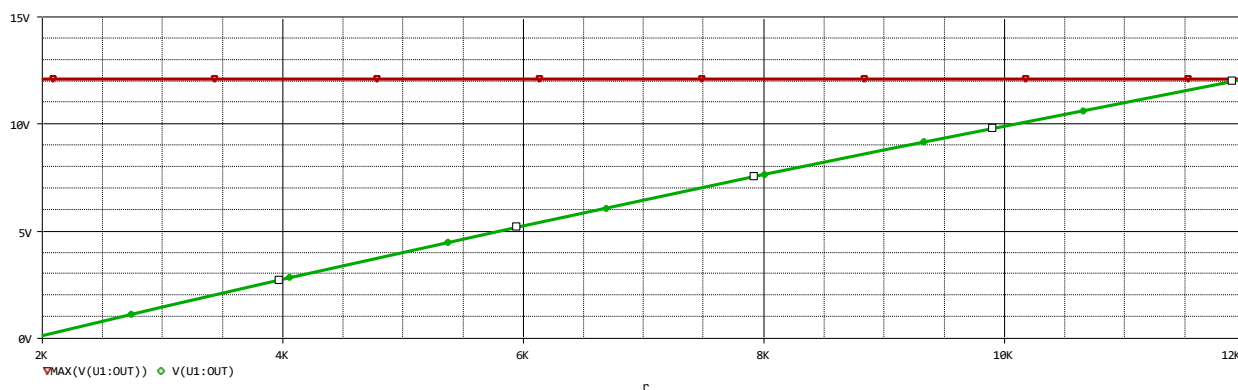În urma simulării se observă ca am o variație de tensiune între  $[0 - (V_{CC}-2V)]$  și anume  $[0-12V]$


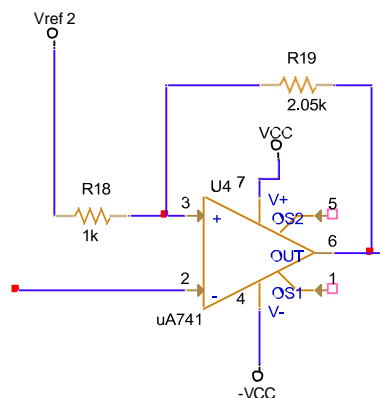
## 9. Comparator neinversor

Sistemul se va proiecta astfel încât ca la atingerea nivelului de fum de 1500 [ppm] led-ul să se aprinda iar la atingerea nivelului de fum de 1150 led-ul să se stingă. O să realizez acest lucru folosind un comparator neinversor



Calculule

$$R_{\text{sensor}} \in [2K - 12K]$$

Rezistenta variaza 10K

Presiunea variaza 440ppm

$$\frac{10K}{440ppm} = \frac{10 \times 10^3 Ohm}{440ppm}$$

$$\Rightarrow 22.72 Ohm/ppm$$

$$R1 = 2K + 40ppm \times \frac{22,72}{ppm} = 2K + 908,8m = 2,908K$$

$$R2 = 12K - 50ppm \times \frac{22,72}{ppm} = 12K - 1,136K = 10,864K$$

$$V \in [0,12V] \Rightarrow \text{Variază } 12 V$$

$$\frac{12V}{440m} = \frac{0.027V}{ppm}$$

$$0.027V \dots 1ppm$$

$$x \dots 40ppm$$

$$x = \frac{40ppm \times 0.027V}{1ppm} = 1,09V$$

$$0.027V \dots 1ppm$$

$$y \dots 390ppm$$

$$y = 10,53V$$

$$V_{PH}=10,86V \rightarrow 1500 \text{ [ppm]}$$

$$V_{PL}=2,90V \rightarrow 1150 \text{ [ppm]}$$

$$V_{PH} = -\frac{R_{18}}{R_{18}+R_{19}} \times V_{cc} + \frac{R_{19}}{R_{18}+R_{19}} \times V_{ref} \quad (6)$$

$$V_{PL} = \frac{R_{18}}{R_{18}+R_{19}} \times V_{cc} + \frac{R_{19}}{R_{18}+R_{19}} \times V_{ref} \quad (7)$$

Am scăzut cele două ecuații =>

$$V_{PH} - V_{PL} = 2 \times V_{cc} \times \frac{R_{18}}{R_{18}+R_{19}} \quad (8)$$

$$10,53 - 1,09 = 2 \times 14 \times \frac{R_{18}}{R_{18} + R_{19}}$$

$$9,44 = 28 \times \frac{R_{18}}{R_{18} + R_{19}}$$

$$\frac{R_{18}}{R_{18} + R_{19}} = \frac{9,44}{28}$$

$$\frac{R_{18}}{R_{18} + R_{19}} = 0,33$$

$$R18 = 0,33 \times R18 + 0,33 \times R19$$

$$0,67 \times R18 = 0,33 \times R19$$

$$\frac{R19}{R18} = \frac{0,67}{0,33}$$

$$\frac{R19}{R18} = 2,03$$

Am ales  $R18=1K$

$$R19=2,03K \rightarrow 2,05K$$

E96 1%

Am adunat cele 2 ecuatii =>

$$V_{PH} + V_{PL} = 2 \times \frac{R2}{R1+R2} \times V_{ref} \quad (9)$$

$$11,62 = 2 \times \frac{2,03}{3,03} \times V_{ref} \quad (10)$$

$$11,62 = 1,33 \times V_{ref}$$

$$V_{ref} = 8,67V$$

$$V_{ref} = \frac{R20}{R20+R21} \times V_{CC} \quad (11)$$

$$8,67 = \frac{R20}{R20+R21} \times 14 \quad (12)$$

$$\frac{R20}{R20 + R21} = 0,61$$

$$R21 = 0,61 \times R20 + 0,61 \times R21$$

$$0,39 \times R21 = 0,61 \times R20$$

$$\frac{R21}{R20} = \frac{0,61}{0,39}$$


$$\frac{R21}{R20} = 1,56k$$

Am ales  $R20=1K$

$$\Rightarrow R_{21}=1,56k \rightarrow 1,58K$$


E96 1%

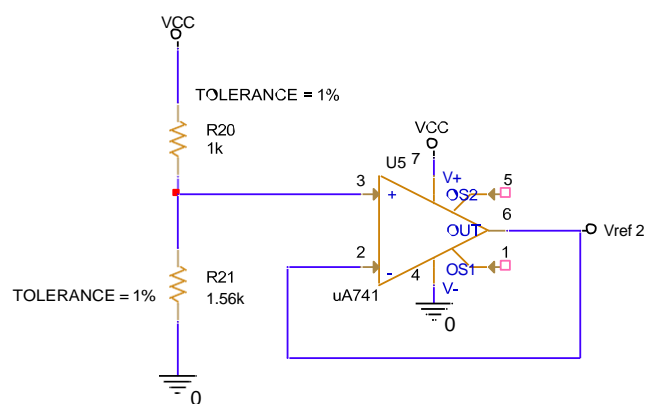Am realizat încă un divizor de tensiune pentru Vref 2.




După cum se poate observa, pentru concentrația fumului de 1500 se aprinde alarma

$$V_{PH}=10,86V$$

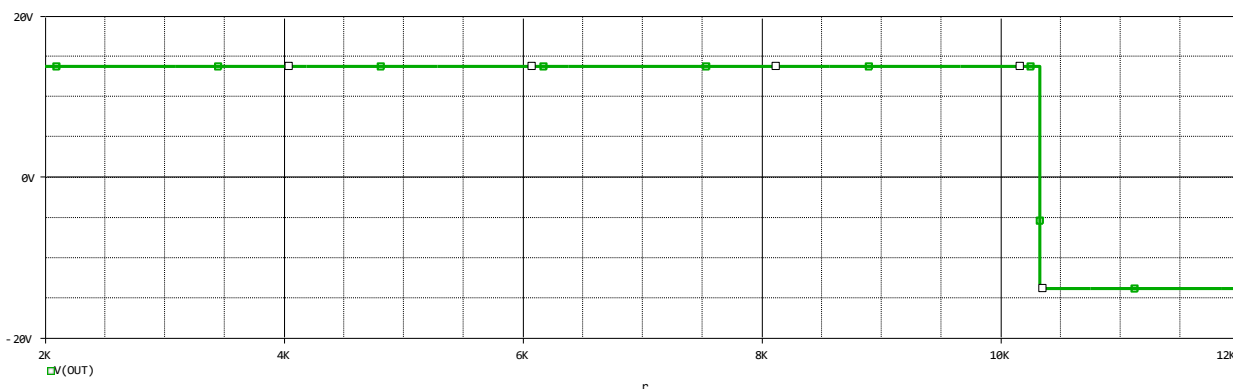

Dupa cum se poate observa, pentru concentrația fumului de 1150 se stinge alarma

$$V_{PL}=2,90V$$

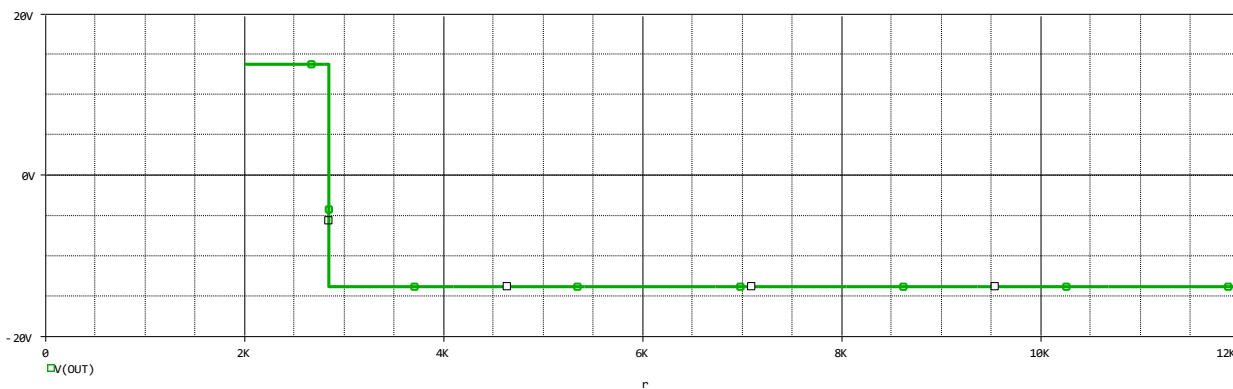

## 10. LED-ul si rezistența

M-am uitat in foaia de catalog a led-ului roșu

## Standard LED


### Red Emitting Colour



#### Features:

- High intensity
- Standard T-1 3/4 diameter package
- General purpose leads
- Reliable and rugged

#### Package Dimensions:

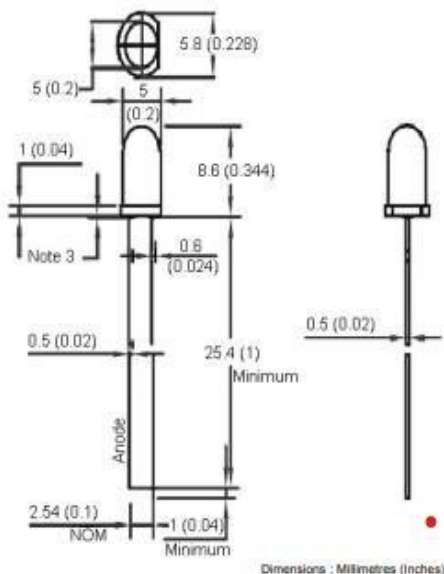

#### Specification Table

Chip Material	Lens Colour	Source Colour	Part Number
AlGaAs	Diffused	Red	MV5754A

#### Notes:

1. Tolerance is  $\pm 0.25$  mm (0.01") unless otherwise noted
2. Protruded resin under flange is 1 mm (0.04") maximum
3. Lead spacing is measured where the leads emerge from the package

www.element14.com  
www.farnell.com  
www.newark.com





## Standard LED

### Red Emitting Colour



Absolute Maximum Ratings at  $T_a = 25^\circ\text{C}$

Parameter	Maximum	Unit
Power Dissipation	80	mW
Peak Forward Current (1/10 Duty Cycle, 0.1 ms Pulse Width)	100	mA
Continuous Forward Current	20	
Derating Linear From $50^\circ\text{C}$	0.4	$\text{mA} / ^\circ\text{C}$
Reverse Voltage	5	V
Operating Temperature Range	$-25^\circ\text{C}$ to $+80^\circ\text{C}$	
Storage Temperature Range	$-40^\circ\text{C}$ to $+100^\circ\text{C}$	
Lead Soldering Temperature (4 mm (0.157) Inches from Body)	260 $^\circ\text{C}$ for 5 s	

Electrical Optical Characteristics at  $T_a = 25^\circ\text{C}$

Parameter	Symbol	Minimum	Typical	Maximum	Unit	Test Condition
Luminous Intensity	$I_v$		40		mcad	$I_f = 20 \text{ mA}$ (Note 1)
Viewing Angle	$2\theta_{1/2}$		25		Deg	(Note 2)
Peak Emission Wavelength	$\lambda_p$		640		nm	$I_f = 20 \text{ mA}$
Dominant Wavelength	$\lambda_d$		635		nm	$I_f = 20 \text{ mA}$ (Note 3)
Spectral Line Half-Width	$\Delta\lambda$		25		nm	$I_f = 20 \text{ mA}$
Forward Voltage	$V_f$		2	2.5	V	$I_f = 20 \text{ mA}$
Reverse Current	$I_R$	-	-	100	$\mu\text{A}$	$V_R = 5 \text{ V}$

Notes:


1. Luminous intensity is measured with a light sensor and filter combination that approximates the CIE eye-response curve
2.  $\theta_{1/2}$  is the off-axis angle at which the luminous intensity is half the axial luminous intensity
3. The dominant wavelength ( $\lambda_d$ ) is derived from the CIE chromaticity diagram and represents the single wavelength which defines the colour of the device

## Standard LED

### Red Emitting Colour

**multicomp**


#### Typical Characteristics

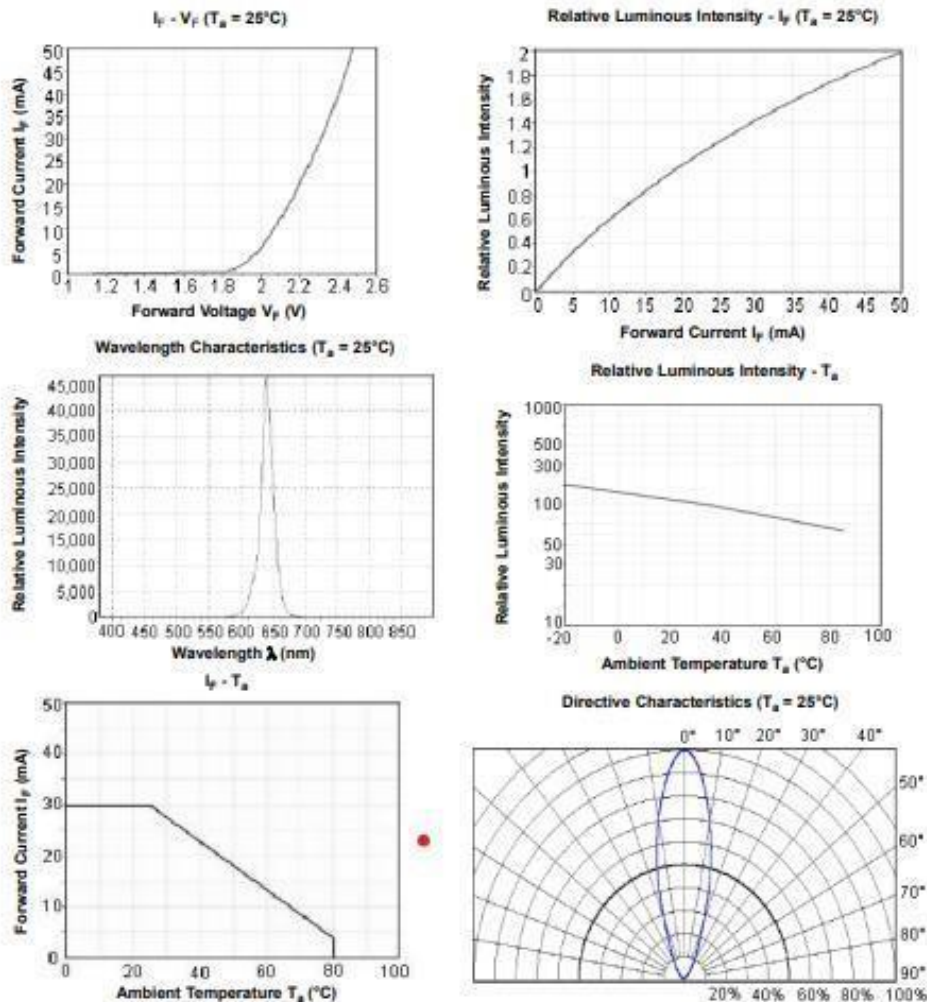

**Important Notice:** This data sheet and its contents (the "Information") belong to the members of the Premier Farnell group of companies (the "Group") or are licensed to it. No licence is granted for the use of it other than for information purposes in connection with the products to which it relates. No licence of any intellectual property rights is granted. The Information is subject to change without notice and replaces all data sheets previously supplied. The Information supplied is believed to be accurate but the Group assumes no responsibility for its accuracy or completeness, any error in or omission from it or for any use made of it. Users of this data sheet should check for themselves the information and the suitability of the products for their purpose and not make any assumptions based on information included or omitted. Liability for loss or damage resulting from any reliance on the information or use of it (including liability resulting from negligence or where the Group was aware of the possibility of each loss or damage arising) is excluded. This will not operate to limit or restrict the Group's liability for death or personal injury resulting from its negligence. Multicomp is the registered trademark of the Group. © Premier Farnell plc 2011.

[www.element14.com](http://www.element14.com)  
[www.farnell.com](http://www.farnell.com)  
[www.newark.com](http://www.newark.com)

**multicomp**

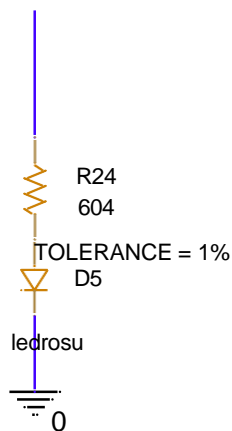


Din foaia de catalog  $\Rightarrow I_{led} \cong 30mA$

$$R8 = \frac{E - V_{led}}{I_{led}} = \frac{20V - 2V}{30mA} = \frac{18V}{30mA} = 0.6 \times 10^3 \Omega = 600 \Omega \rightarrow 604 \Omega$$

E96 1%

Pentru a ridica caracteristica LED-ului roșu o să mă folosesc de foaia de catalog a acestuia.

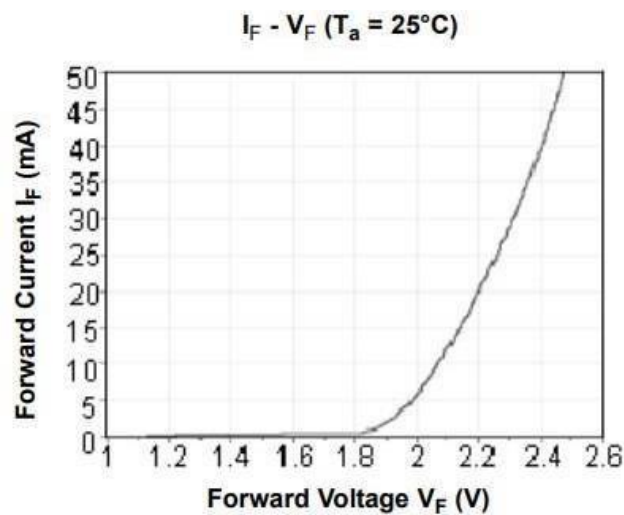În cadrul foii de catalog, sunt expuse mai multe caracteristici cea de mai jos e cea mai utilă în cazul meu deoarece arată modul în care variază curentul prin LED în funcție de tensiune.




Observăm faptul ca tensiunea de prag a LED-ului roșu este in jur de 2V.

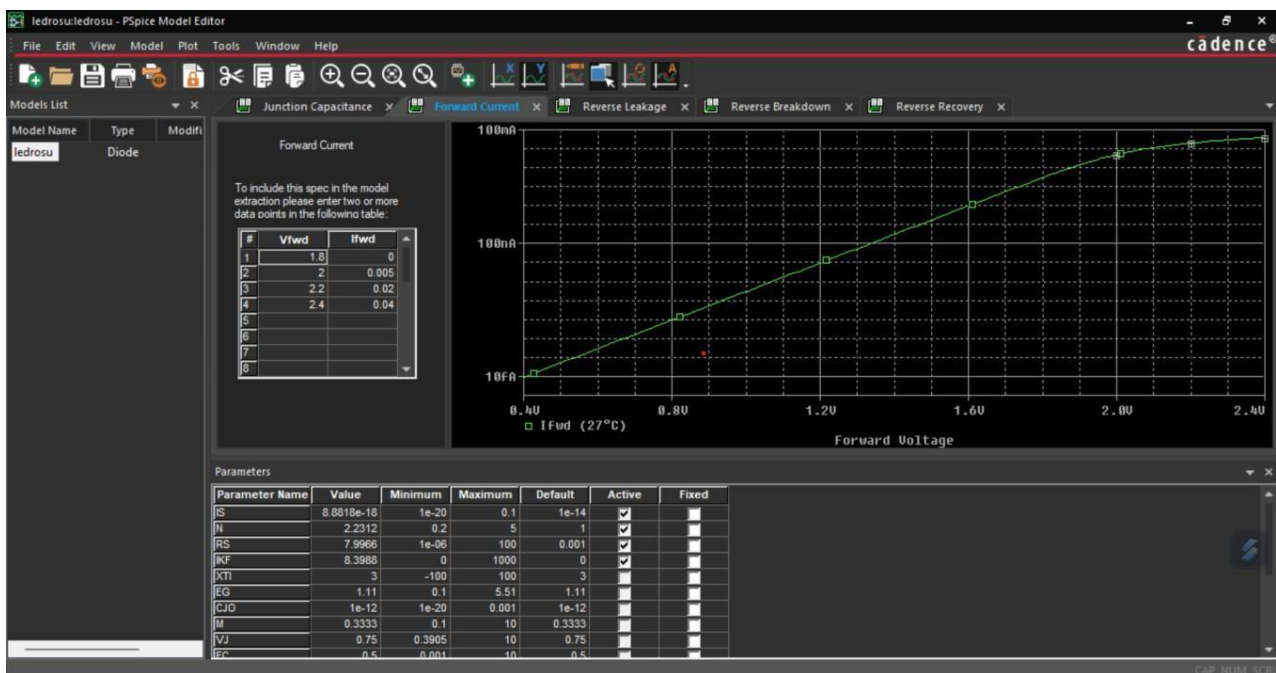
## Modelare LED

Pentru a modela LED-ul am folosit Pspice Model Editor.

Am adăugat valorile in urma analizei caracteristicii de mai sus



Am extras parametrii

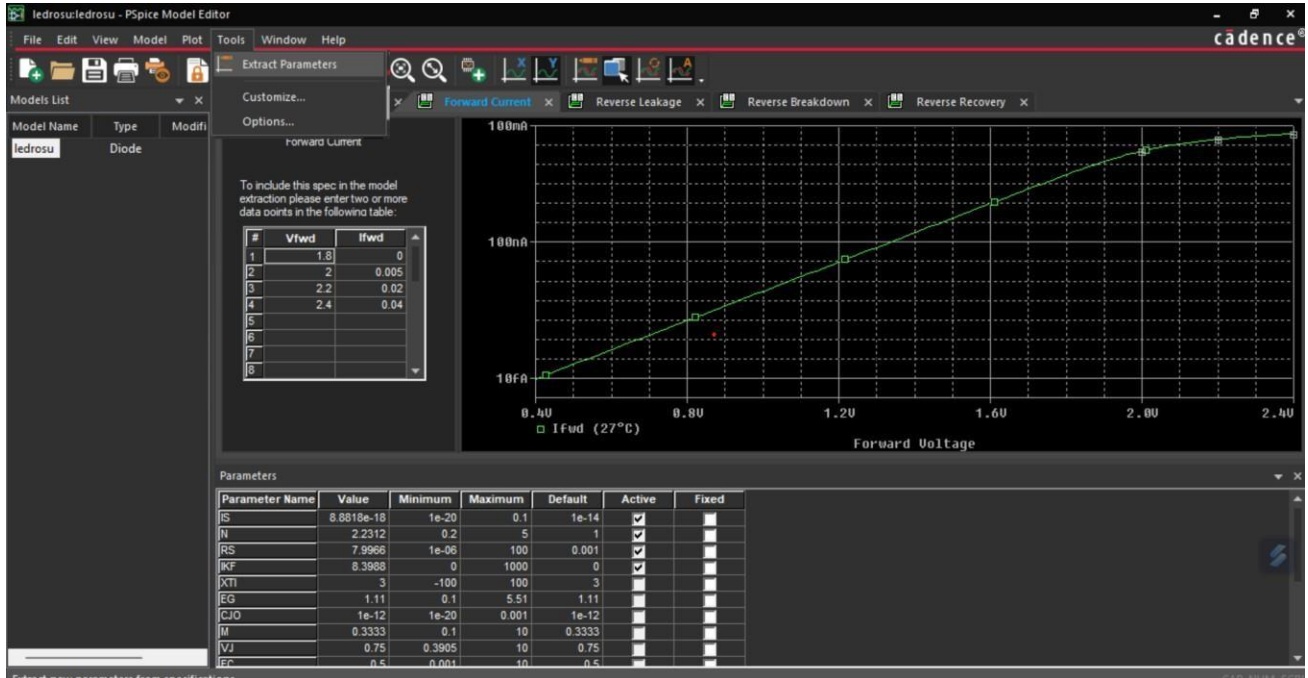

```



*BeginSpec
*IF: (1.8000,0) (2,5.0000E-3) (2.2000,20.000E-3) (2.4000,40.000E-3)
*JC:
*RL:
*RB: Vz=0 Iz=0 Zz=0
*RR: Trr=0 Ifwd=10.000E-3 Irev=10.000E-3 Rl=100
*EndSpec

*BeginTrace
*IF: 1,0,.4,2.4000,1,3,0,0,-1 (27)
*JC: 0,1,.1,10,1,3,0,0,-1 (27)
*RL: 0,0,1,100,1,3,0,0,-1 (27)
*RB: 0,1,100.00E-6,1,1,3,0,0,-1 (27)
*RR: 0,0,-5.0000E-9,20.000E-9,1,3,0,0,-1 (27)
*EndTrace

*BeginParam
*IS=8.8818E-18 (10.000E-21,.1,0)
*N=2.2312 (.2,5,0)
*RS=7.9966 (1.0000E-6,100,0)
*IKF=8.3988 (0,1.0000E3,0)
*XTI=3 (-100,100,0)
*EG=1.1100 (.1,5.5100,0)
*CJO=1.0000E-12 (10.000E-21,1.0000E-3,0)
*M= .3333 ( .1 10 0)



```

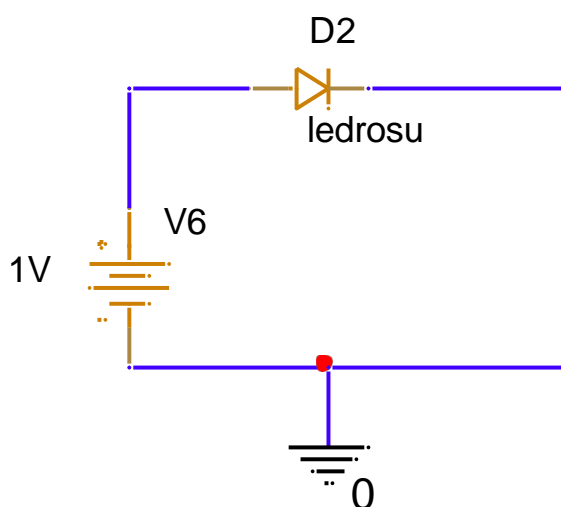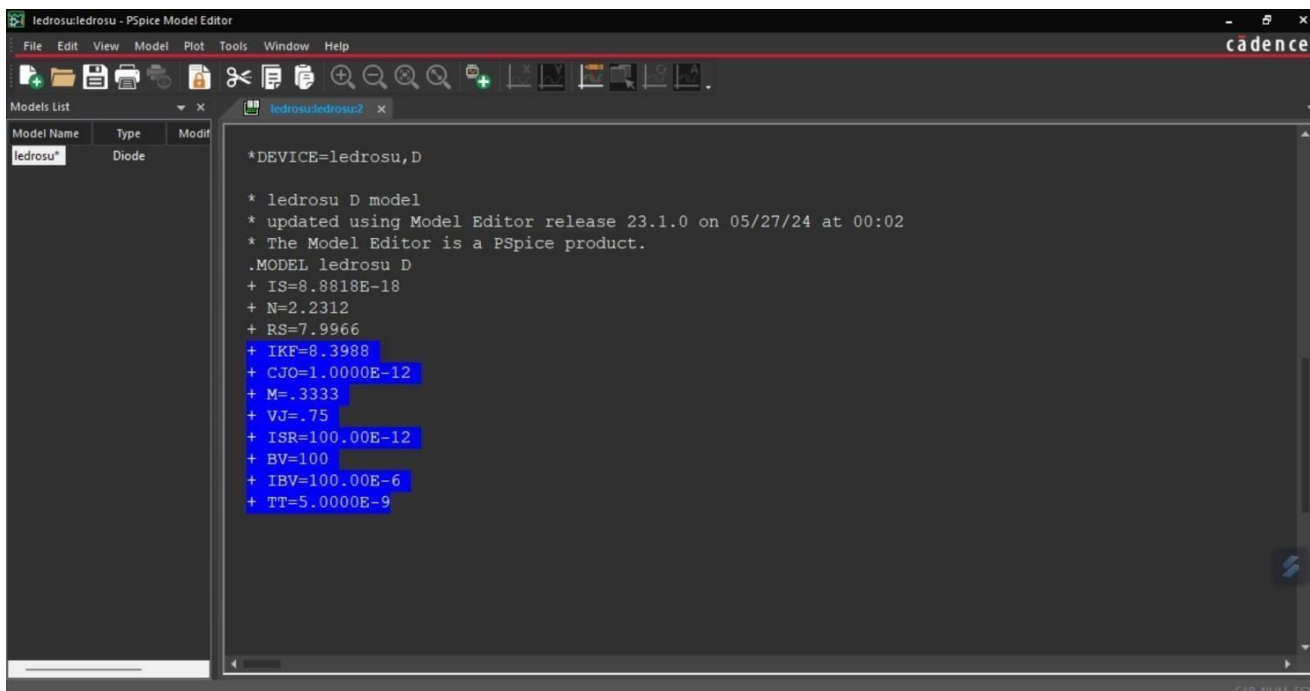Am șters tot de la Rs în jos iar apoi l-am salvat cu numele "ledrosu"






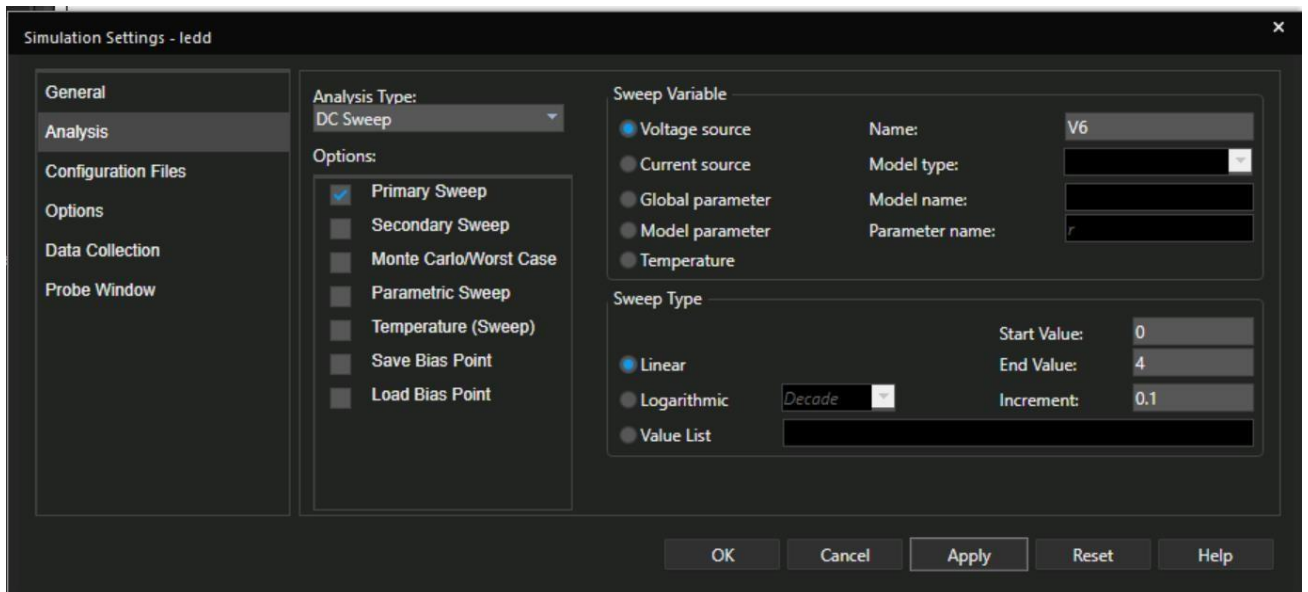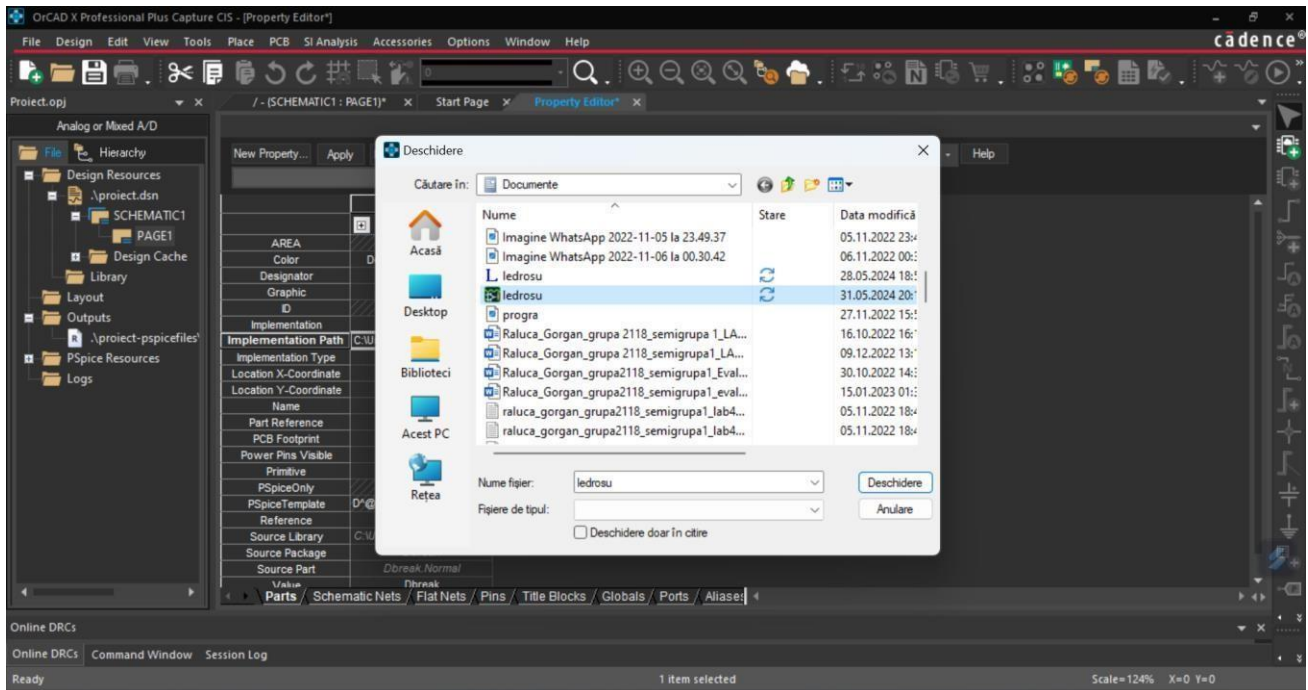Punem în proiectul Orcad unde este circuitul o componentă Dbreak. Dăm click dreapta pe această componentă și la Implementation Path ne punem fișierul .lib creat în model editor.





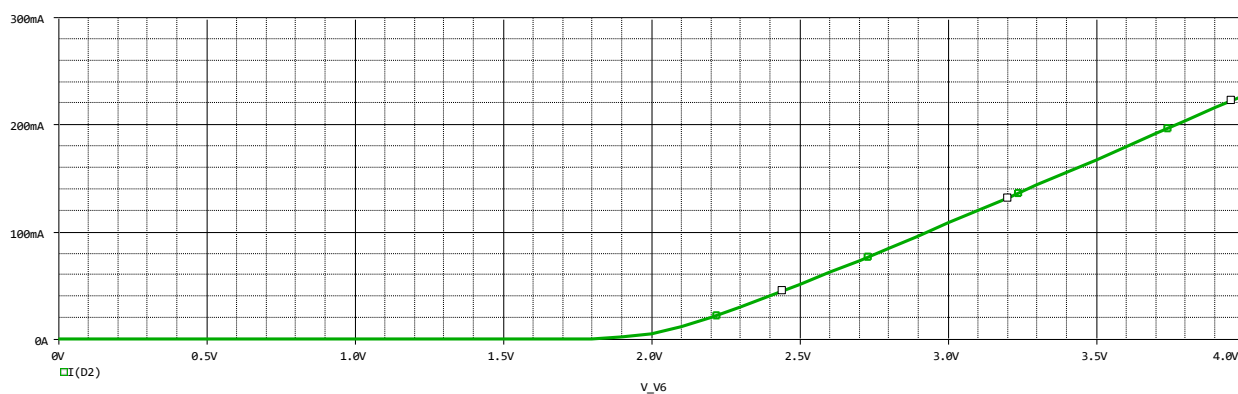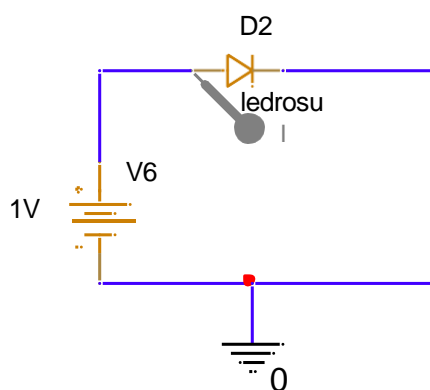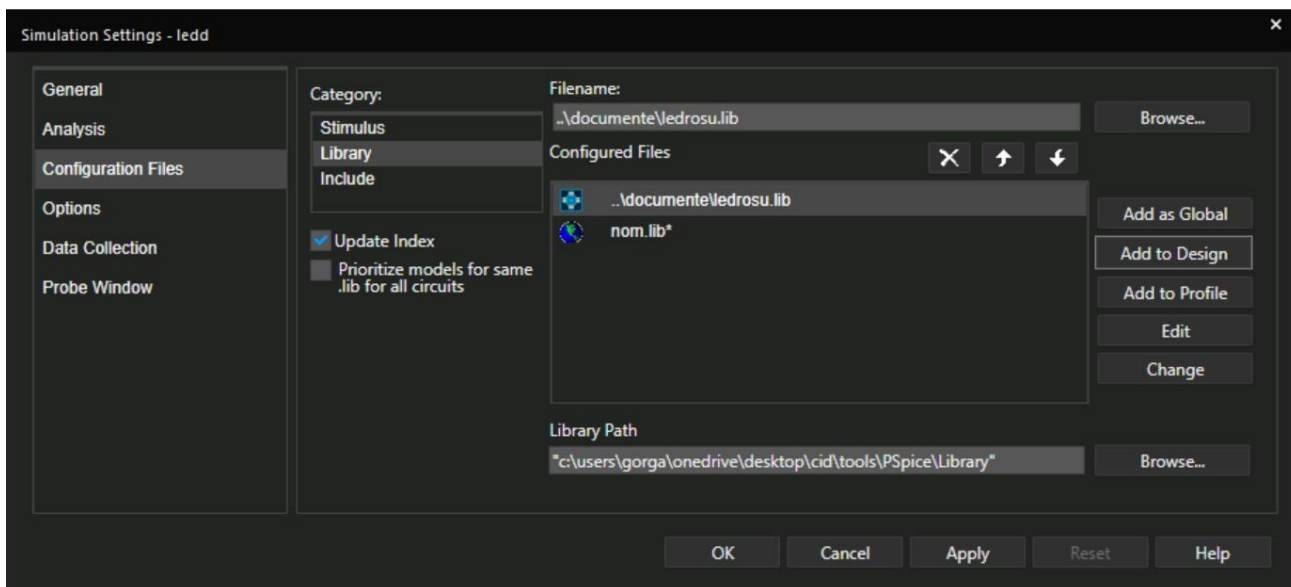Dăm la Configuration Files->Library si adăugăm fișierul .lib, apoi apăsăm Add to Design, apoi Apply și Ok.






## 11. Releul

Am ales un tranzistor npn de tip BC107A, urmărind foaia de catalog a acestuia.

BC107,A,B  
BC108B,C  
BC109B,C

**NPN SILICON TRANSISTOR**



**TO-18 CASE**

**Central**  
Semiconductor Corp.

www.centraisemi.com

**DESCRIPTION:**  
The CENTRAL SEMICONDUCTOR BC107, BC108, BC109 series types are small signal NPN silicon transistors, manufactured by the epitaxial planar process, designed for general purpose amplifier applications.

**MARKING: FULL PART NUMBER**

MAXIMUM RATINGS: (T <sub>A</sub> =25°C)		SYMBOL	BC107	BC108	BC109	UNITS
Collector-Base Voltage	V <sub>CB</sub>	V <sub>CB</sub>	50	30	30	V
Collector-Emitter Voltage	V <sub>CE</sub>	V <sub>CE</sub>	45	25	25	V
Emitter-Base Voltage	V <sub>EB</sub>	V <sub>EB</sub>	6.0	5.0	5.0	V
Continuous Collector Current	I <sub>C</sub>	I <sub>C</sub>		200		mA
Power Dissipation	P <sub>D</sub>	P <sub>D</sub>		600		mW
Operating and Storage Junction Temperature	T <sub>J</sub> , T <sub>slg</sub>	T <sub>J</sub> , T <sub>slg</sub>		-65 to +200		°C
Thermal Resistance	θ <sub>JC</sub>	θ <sub>JC</sub>		175		°C/W

ELECTRICAL CHARACTERISTICS: (T <sub>A</sub> =25°C unless otherwise noted)		SYMBOL	TEST CONDITIONS	MIN	TYP	MAX	UNITS
I <sub>CBO</sub>	V <sub>CB</sub> =45V (BC107)	I <sub>CBO</sub>				15	nA
I <sub>CBO</sub>	V <sub>CB</sub> =45V, T <sub>A</sub> =125°C (BC107)	I <sub>CBO</sub>				4.0	μA
I <sub>CBO</sub>	V <sub>CB</sub> =25V (BC108, BC109)	I <sub>CBO</sub>				15	nA
I <sub>CBO</sub>	V <sub>CB</sub> =25V, T <sub>A</sub> =125°C (BC108, BC109)	I <sub>CBO</sub>				4.0	μA
BV <sub>CEO</sub>	I <sub>C</sub> =2.0mA (BC107)	BV <sub>CEO</sub>		45			V
BV <sub>CEO</sub>	I <sub>C</sub> =2.0mA (BC108, BC109)	BV <sub>CEO</sub>		25			V
BV <sub>EBO</sub>	I <sub>E</sub> =10μA (BC107)	BV <sub>EBO</sub>		6.0			V
BV <sub>EBO</sub>	I <sub>E</sub> =10μA (BC108, BC109)	BV <sub>EBO</sub>		5.0			V
V <sub>CE</sub> (SAT)	I <sub>C</sub> =10mA, I <sub>B</sub> =0.5mA	V <sub>CE</sub> (SAT)				0.25	V
V <sub>CE</sub> (SAT)	I <sub>C</sub> =100mA, I <sub>B</sub> =5.0mA	V <sub>CE</sub> (SAT)				0.6	V
V <sub>BE</sub> (SAT)	I <sub>C</sub> =10mA, I <sub>B</sub> =0.5mA	V <sub>BE</sub> (SAT)			0.7	0.83	V
V <sub>BE</sub> (SAT)	I <sub>C</sub> =100mA, I <sub>B</sub> =5.0mA	V <sub>BE</sub> (SAT)			1.0	1.05	V
V <sub>BE</sub> (ON)	V <sub>CE</sub> =5.0V, I <sub>C</sub> =2.0mA	V <sub>BE</sub> (ON)		0.55		0.7	V
V <sub>BE</sub> (ON)	V <sub>CE</sub> =5.0V, I <sub>C</sub> =10mA	V <sub>BE</sub> (ON)				0.77	V
h <sub>FE</sub>	V <sub>CE</sub> =5.0V, I <sub>C</sub> =10μA (BC107B, BC108B, BC109B)	h <sub>FE</sub>		40			
h <sub>FE</sub>	V <sub>CE</sub> =5.0V, I <sub>C</sub> =10μA (BC108C, BC109C)	h <sub>FE</sub>		100			
h <sub>FE</sub>	V <sub>CE</sub> =5.0V, I <sub>C</sub> =2.0mA (BC107)	h <sub>FE</sub>		110		450	
h <sub>FE</sub>	V <sub>CE</sub> =5.0V, I <sub>C</sub> =2.0mA (BC107A)	h <sub>FE</sub>		110		220	
h <sub>FE</sub>	V <sub>CE</sub> =5.0V, I <sub>C</sub> =2.0mA (BC107B, BC108B, BC109B)	h <sub>FE</sub>		200		450	
h <sub>FE</sub>	V <sub>CE</sub> =5.0V, I <sub>C</sub> =2.0mA (BC108C, BC109C)	h <sub>FE</sub>		420		800	

R1 (16-August 2012)


BC107,A,B  
BC108B,C  
BC109B,C  
  
NPN SILICON TRANSISTOR

**Central**  
Semiconductor Corp.

ELECTRICAL CHARACTERISTICS - Continued: ( $T_A=25^\circ\text{C}$  unless otherwise noted)

SYMBOL	TEST CONDITIONS	MIN	TYP	MAX	UNITS
$\eta_{fe}$	$V_{CE}=5.0\text{V}$ , $I_C=2.0\text{mA}$ , $f=1.0\text{kHz}$ (BC107)	125		500	
$\eta_{fe}$	$V_{CE}=5.0\text{V}$ , $I_C=2.0\text{mA}$ , $f=1.0\text{kHz}$ (BC107A)	125		260	
$\eta_{fe}$	$V_{CE}=5.0\text{V}$ , $I_C=2.0\text{mA}$ , $f=1.0\text{kHz}$ (BC107B, BC108B, BC109B)	240		500	
$\eta_{fe}$	$V_{CE}=5.0\text{V}$ , $I_C=2.0\text{mA}$ , $f=1.0\text{kHz}$ (BC108C)		500		
$\eta_{fe}$	$V_{CE}=5.0\text{V}$ , $I_C=2.0\text{mA}$ , $f=1.0\text{kHz}$ (BC109C)	450		900	
$f_T$	$V_{CE}=5.0\text{V}$ , $I_C=10\text{mA}$ , $f=100\text{MHz}$	150			MHz
$C_{ob}$	$V_{CB}=10\text{V}$ , $I_E=0$ , $f=1.0\text{MHz}$			4.5	pF
NF	$V_{CE}=5.0\text{V}$ , $I_C=0.2\text{mA}$ , $R_G=2.0\text{k}\Omega$ , $B=200\text{Hz}$ , $f=1.0\text{kHz}$ (BC107, BC108)			10	dB
NF	$V_{CE}=5.0\text{V}$ , $I_C=0.2\text{mA}$ , $R_G=2.0\text{k}\Omega$ , $B=200\text{Hz}$ , $f=1.0\text{kHz}$ (BC109)			4.0	dB

#### TO-18 CASE - MECHANICAL OUTLINE

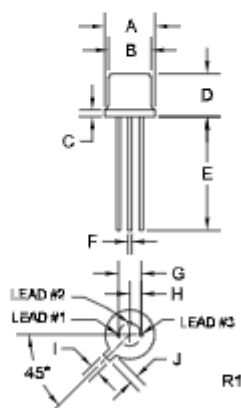

SYMBOL	DIMENSIONS			
	INCHES		MILLIMETERS	
	MIN	MAX	MIN	MAX
A (DIA)	0.209	0.230	5.31	5.84
B (DIA)	0.178	0.195	4.52	4.95
C	-	0.030	-	0.76
D	0.170	0.210	4.32	5.33
E	0.500	-	12.70	-
F (DIA)	0.016	0.019	0.41	0.48
G (DIA)	0.100	-	2.54	-
H	-	0.050	-	1.27
I	0.036	0.046	0.91	1.17
J	0.028	0.048	0.71	1.22

TO-18 (REV: R1)

#### LEAD CODE:


- 1) Emitter
- 2) Base
- 3) Collector

#### MARKING:

FULL PART NUMBER

R1 (16-August 2012)

www.centralsemi.com

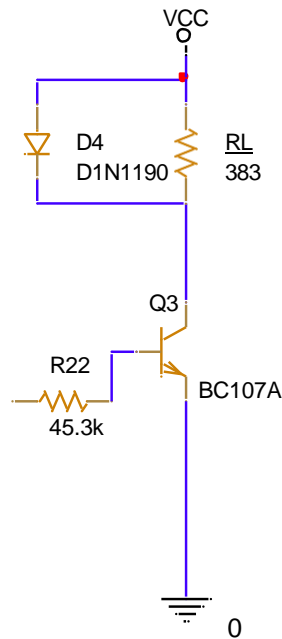

Am ales factorul de amplificare in curent:  $\beta=100$

$V_{cc}=14V$     $V_{CEmin}=2V$     $V_{BE}=0,65V$

$I_{releu}=30mA=I_C=I_E$

$$R_L = \frac{V_{cc} - (V_{CE} + V_{BE})}{I_{releu}} \Rightarrow R_L = \frac{14V - (2V + 0,65V)}{30mA}$$

$$\frac{14V - 2,65V}{30mA} = \frac{11,35V}{30mA} = 0,378 \times 10^3 \text{ Ohm} = 378 \text{ Ohm} \rightarrow 383 \text{ Ohm}$$

E96 1%

$$I_C = \beta \times I_B \Rightarrow I_B = \frac{I_C}{\beta} \Rightarrow I_B = \frac{30mA}{100} = 0,3mA = 300\mu A$$

$$R_9=R_9 = \frac{V_{cc}-V_{BE}}{I_B} = \frac{14V-0,65V}{300\mu A} = \frac{13,35V}{0,3mA} = 44,5 \times 10^3 \text{ Ohm} = 44,5 \text{ KOhm} \rightarrow 44,5 \text{ KOhm}$$

## 12. Analize Monte Carlo/Worst Case


Analiza Monte Carlo constituie cel mai bun mod de analiza a unui circuit din punct de vedere statistic, de a vedea cum se comporta acel circuit la variatii ale valorilor componentelor.


### Analiza Worst-case/Sensitivity

Sensitivity identifică care parametri ai componentelor sunt critici pentru funcționarea circuitului. Această analiză determină în ce măsură fiecare componenta afectează funcționarea circuitului. De asemenea modifică toate valorile pentru a simula cel mai defavorabil caz.


### Analiza Monte Carlo



Facem profilul de simulare


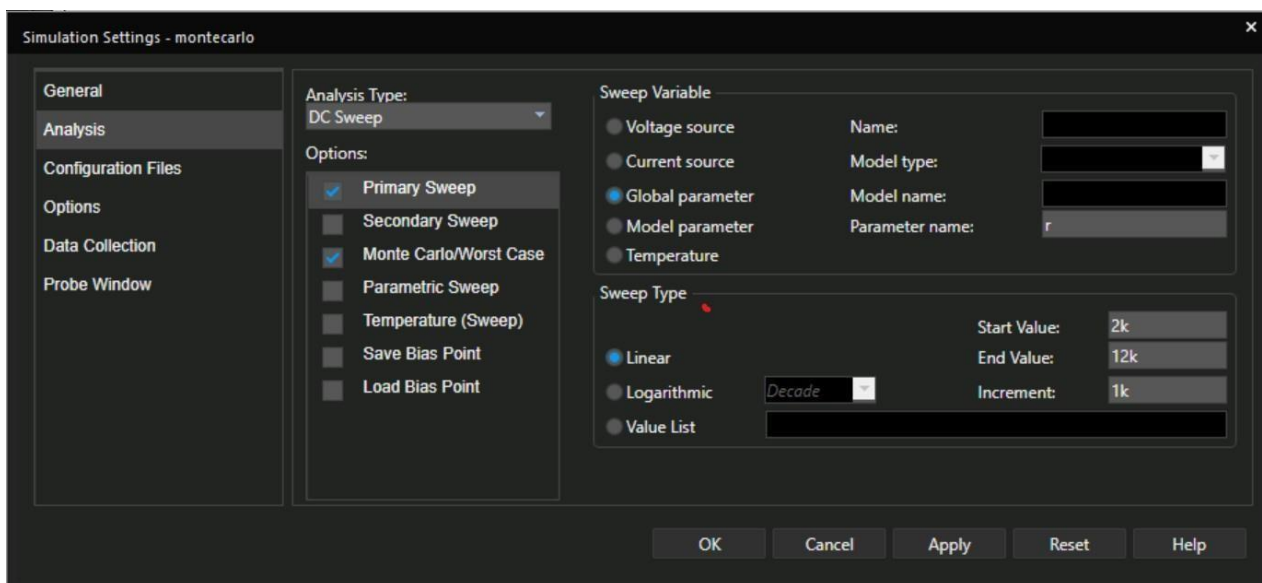


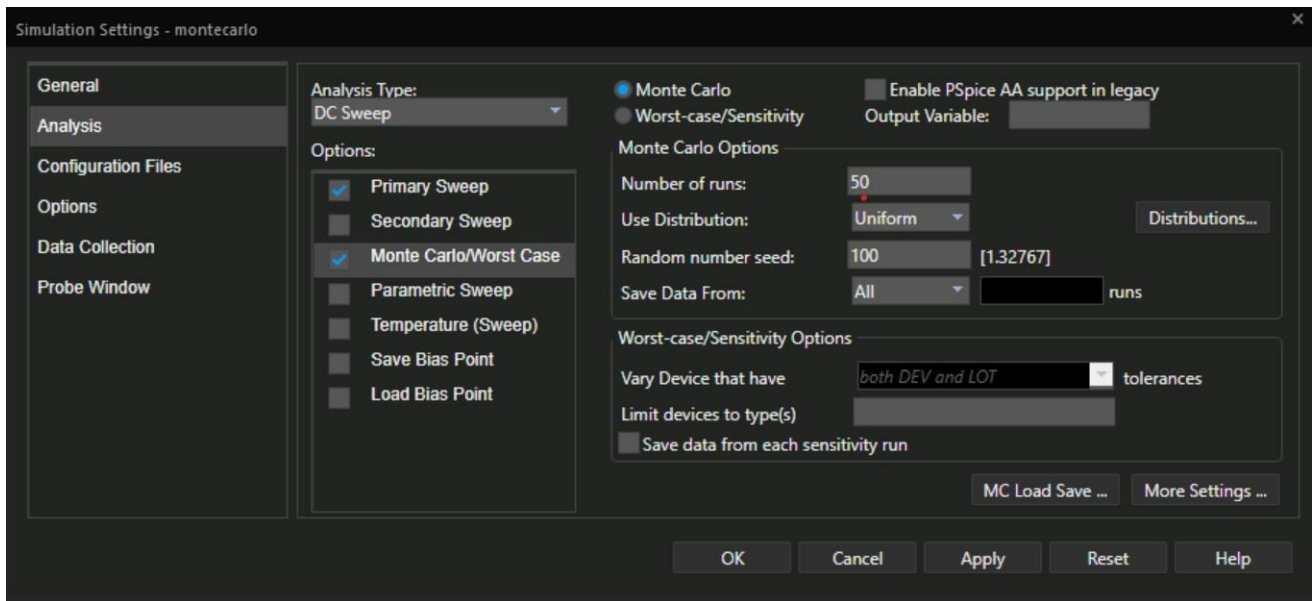

## Simulare

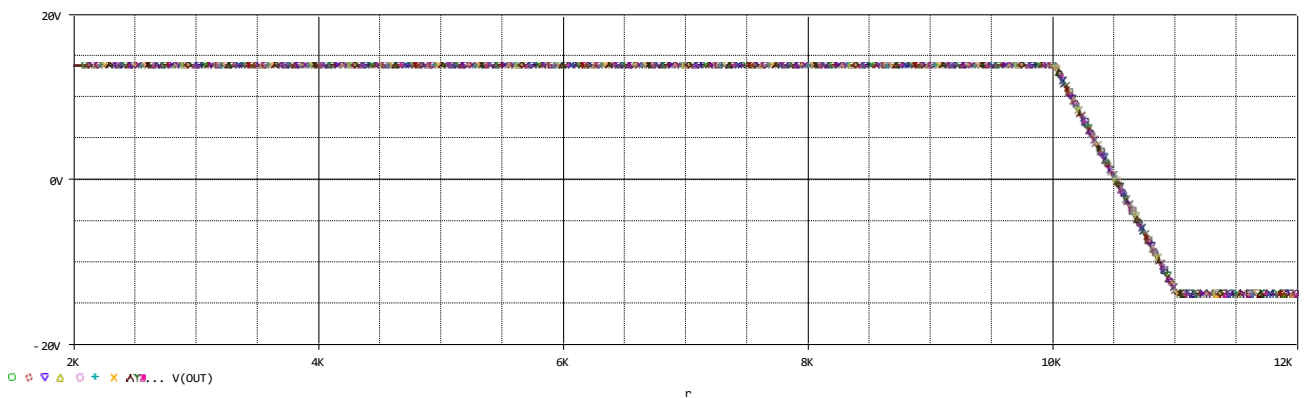

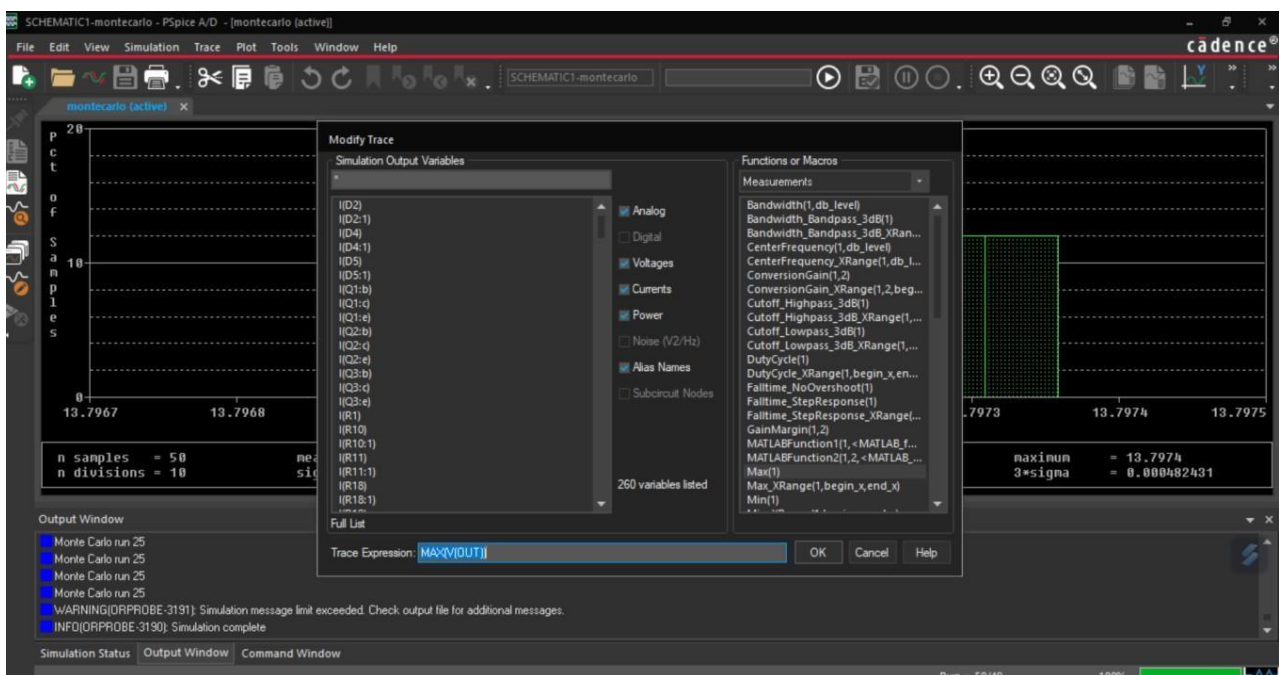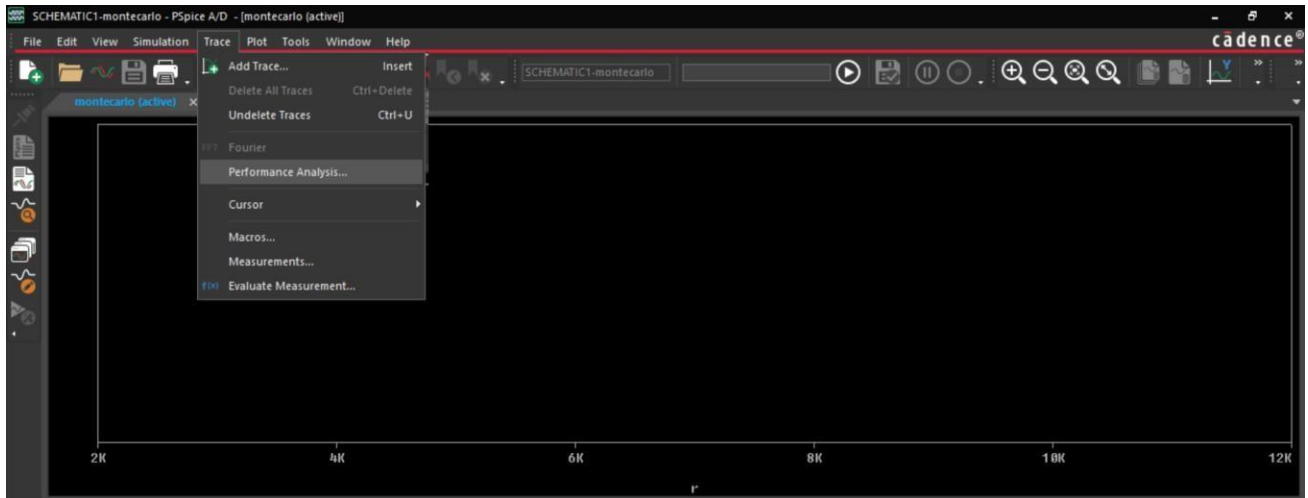

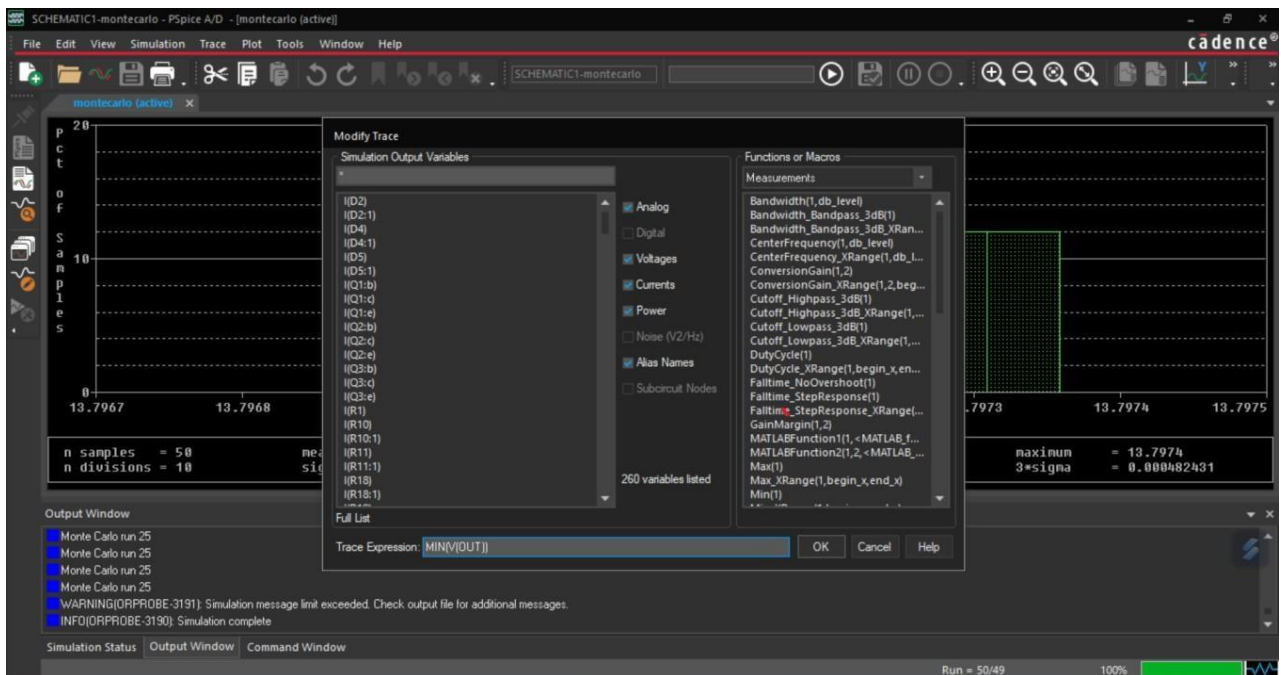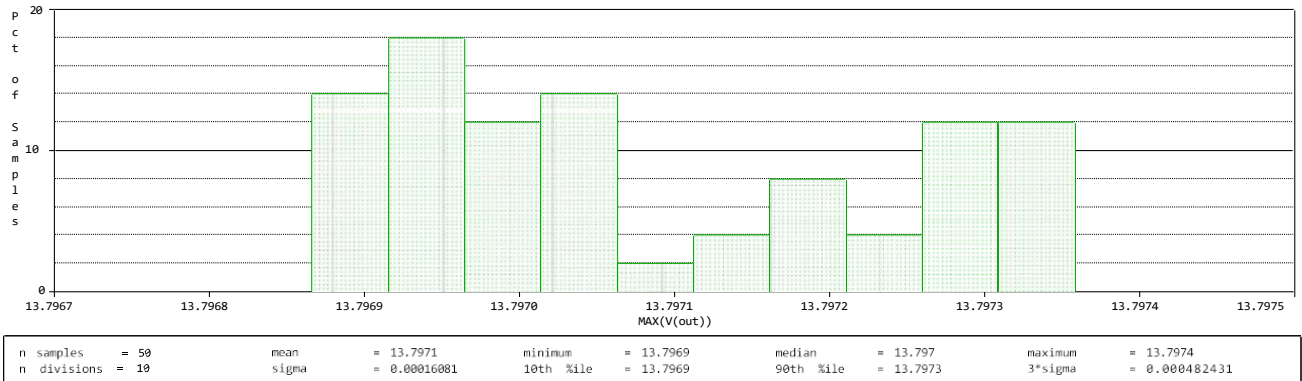





## Analiza Worst-case/Sensitivity

**Simulation Settings - Worstcase**

**General**

**Analysis**

**Configuration Files**

**Options**

**Data Collection**

**Probe Window**

**Analysis Type:** DC Sweep

**Options:**

- ☒ Primary Sweep
- ☐ Secondary Sweep
- ☒ Monte Carlo/Worst Case
- ☐ Parametric Sweep
- ☐ Temperature (Sweep)
- ☐ Save Bias Point
- ☐ Load Bias Point

**Monte Carlo Options**

Number of runs: 50

Use Distribution: Uniform [Distributions...]

Random number seed: 100 [1.32767]

Save Data From: All runs

**Worst-case/Sensitivity Options**

Vary Device that have: both DEV and LOT tolerances

Limit devices to type(s):


☐ Save data from each sensitivity run

MC Load Save ... More Settings ...

OK Cancel Apply Reset Help



## Simulare

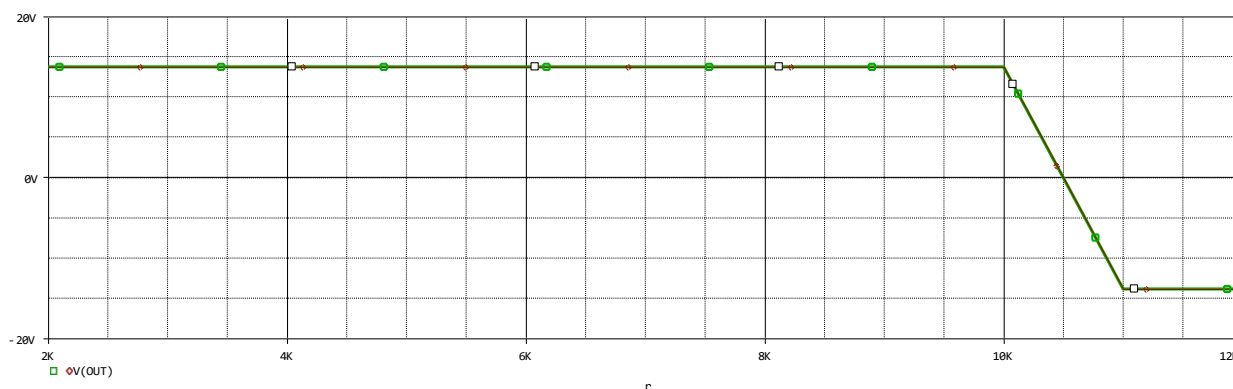

## 13. Bibliografie

### Editare Bibliografie

- Site web [1]
- Foaie de catalog [2]
- Cursuri [3]

### Bibliografie

[1] [https://www.bertys.ro/codul\\_culorilor\\_rezistente.htm](https://www.bertys.ro/codul_culorilor_rezistente.htm)

[2] Tranzistor uA741 , Tranzistor BC107A, Led Roșu

[3] Cursuri Dispozitive Electronice - Prof.dr.ing. Emilia Șipoș

Curs Teams Tehnici CAD- Prof.dr.ing. Ovidiu Pop

[http://193.226.6.189/dce/didactic/de/DE\\_Curs7.pdf](http://193.226.6.189/dce/didactic/de/DE_Curs7.pdf)- [Comparatoare cu AO cu RP. Amplificatoare electronice](#)

[http://193.226.6.189/dce/didactic/de/DE\\_Curs10.pdf](http://193.226.6.189/dce/didactic/de/DE_Curs10.pdf)- [Aplicații cu AO](#)

[http://193.226.6.189/dce/didactic/de/DE\\_Curs13.pdf](http://193.226.6.189/dce/didactic/de/DE_Curs13.pdf)- [TB. Tranzistoare MOS](#)